


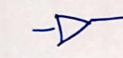
# Digital Logic


## Types of Logic Gates

### Logic Gates


#### Basic Gates


AND  $\Rightarrow$  

OR  $\Rightarrow$  


NOT  $\Rightarrow$  


#### Universal Gates

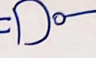NAND  $\Rightarrow$  

NOR  $\Rightarrow$  

#### Arithmetic

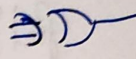XOR  $\Rightarrow$  

X-NOR  $\Rightarrow$  

Input		Output					
A	B	$Y = A \cdot B$	$Y = A + B$	$Y = \overline{A \cdot B}$	$Y = \overline{A + B}$	$Y = A \oplus B$	$Y = \overline{A \oplus B}$
0	0	0	0	1	1	0	1
0	1	0	1	1	0	1	0
1	0	0	1	1	0	1	0
1	1	1	1	0	0	0	1

$NAND \rightarrow NOT + AND$   
 $NOR \rightarrow NOT + OR$

Universal gates  
 we can make any gates  
 from Universal Gates

## Arithmetic Gates

Used in Making Arithmetic Circuits  
 full Adder, Subtractor, half Adder


### NOT Gate

0 - 1

1 - 0

Single Input

A	$\bar{A}$
0	1
1	0

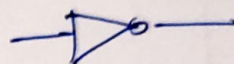


Complement

→ Inverter

### AND Gate

A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

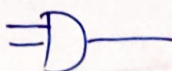

OR


A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1







# Universal Gates

## NAND Gates

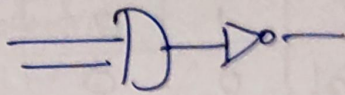

x	y	$P = \overline{A \cdot B}$
0	0	1
1	0	1
0	1	1
1	1	0

## NOR Gate

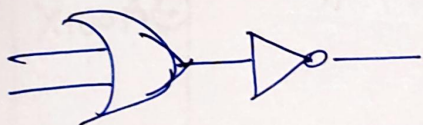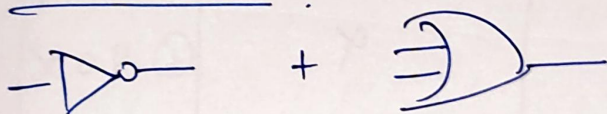


x	y	$P = \overline{x + y}$
0	0	1
1	0	0
0	1	0
1	1	0

## XOR

Exclusive OR

$$A\bar{B} + \bar{A}B$$

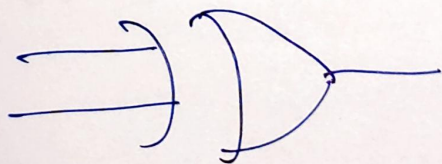

Output is high, if & only if one of the input is high.

A	B	A	$\bar{B}$	$A\bar{B}$	$\bar{A}$	$\bar{A}B$	$\bar{A}B + A\bar{B}$
0	0	0	1	0	1	0	0
0	1	0	0	0	1	1	1
1	0	1	1	1	0	0	1
1	1	1	0	0	0	0	0

Same Input /

Same value  $\rightarrow 0$

$$\boxed{00 \rightarrow 0, 11 \rightarrow 0}$$

$$10 \rightarrow 1, 01 \rightarrow 1$$

A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

$$Y = A \odot B$$

Complement of XOR

A	B	$Y = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

$$AB + \bar{A}\bar{B}$$



Gates  $\rightarrow$  Flip Flops  $\rightarrow$  Registers

## Properties of Various Logic Gates

Gates	Properties		
	Idempotent / Closure	Commutative	Associative
NOT -	X	NA	NA
AND .	✓	✓	✓
OR +	✓	✓	✓
NAND $\uparrow$	X	✓	X
NOR $\downarrow$	X	✓	X
XOR $\oplus$	X	✓	✓
XNOR $\odot$	X	✓	✓

Idempotent / Closure Property  $\rightarrow$   $A \cdot A = A$  and ✓  
 $A = \bar{A}$  Not X

AND OR ] - Idempotent  $A + A = A$  OR ✓

$A \uparrow A =$   
 $\left. \begin{array}{l} \bar{A} \cdot A \\ \bar{A} \end{array} \right\}$  NAND X

Commutative Property



$$A \cdot B = B \cdot A$$

$$0 \cdot 1 = 1 \cdot 0$$

AND

$$0 + 1 = 1 + 0$$

OR

$$\overline{A \cdot B} = \overline{B \cdot A}$$

$$0 \cdot 1 = 1 \cdot 0$$

$$\overline{0} = \overline{0}$$

$$1 = 1$$

AND  
OR  
NOR  
NAND  
XOR  
XNOR

- all gates follow Commutative Property

Associative Property



$$(A \uparrow B) \uparrow C = A \uparrow (B \uparrow C)$$

AND  
OR  
XOR  
XNOR

- Associative Property follow by Every gate Except Universal Gate.

$$\overline{A \cdot B} \neq \overline{A} \cdot \overline{B}$$

$$AB + \overline{C} \neq \overline{A} + BC$$

NOT  
AND  
OR  
XOR  
XNOR

- using NAND & NOR








Implement all gates using NAND & NOR Gates

	NAND	NOR
NOT	1	1
AND	2	3
OR	3	2
XOR	4	5
XNOR	5	4

NAND to NOR  $\rightarrow 4$

NOR to NAND  $\rightarrow 4$

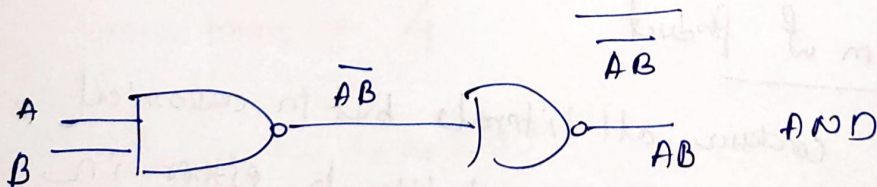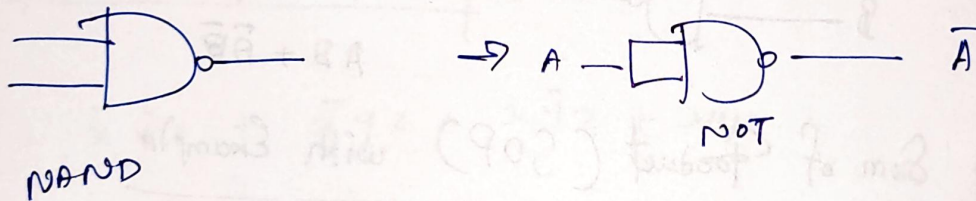

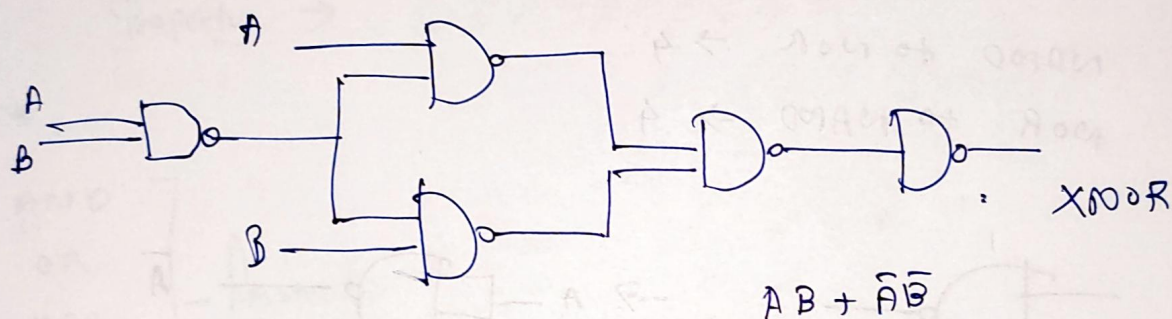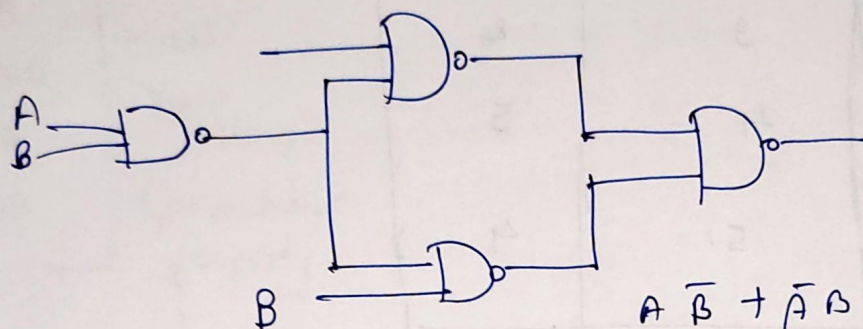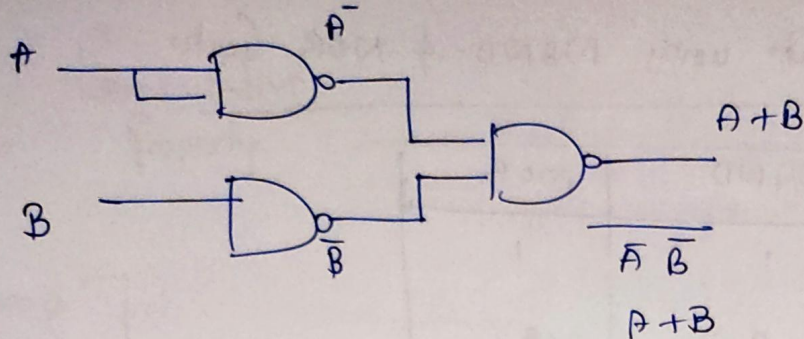

Canonical Sum of Product (SOP) with Example

Canonical Sum of Product

SOP need not contain all literals but in canonical form, Each product term contains all literals either in Complemented or Uncomplemented form.

These product terms are nothing but the minterms.



Sum of all minterms of 'f' for which 'f' assumes 1 is called Canonical SOP or Disjunctive normal form.

$\bar{x}\bar{y}z + x\bar{y}$  Sum of Product terms.

$$x\bar{y}z + x\bar{y} \quad f(x, y, z)$$

	x	y	z	f	
	0	0	0	0	
1	0	0	1	1	✓
	0	1	0	0	
3	0	1	1	1	✓
	1	0	0	0	
5	1	0	1	1	✓
	1	1	0	0	
7	1	1	1	1	✓

$$f = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + x\bar{y}$$

Total  
minterms = 4

$$f = \sum m(1, 3, 5, 7)$$

or

$$f = \sum m_1 + m_3 + m_5 + m_7$$